


2313 666

殷家兴 自动化

数电⑦

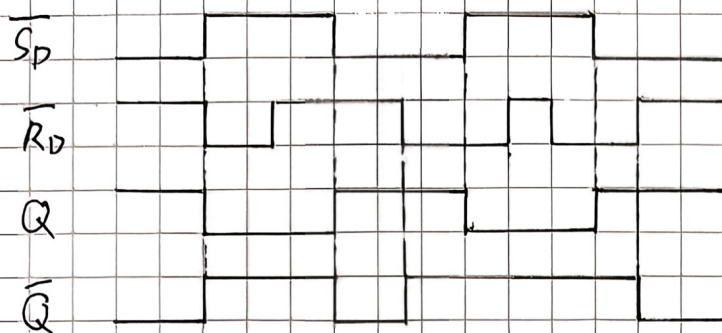
4.4 解:

$$Q_{n+1} = \bar{S} + RQ = \bar{S}_0 + \bar{R}_0 Q = S_0 + \bar{R}_0 Q_n$$




4.6

特解:

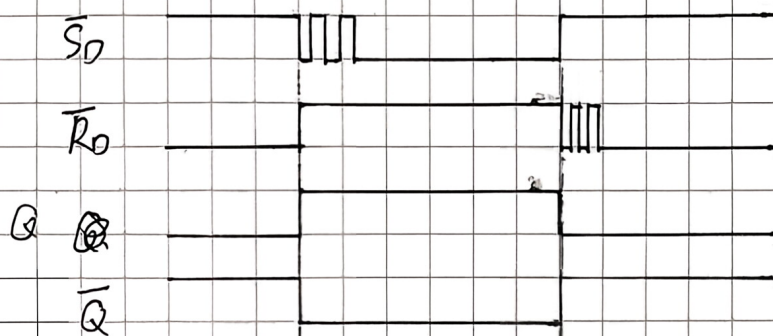

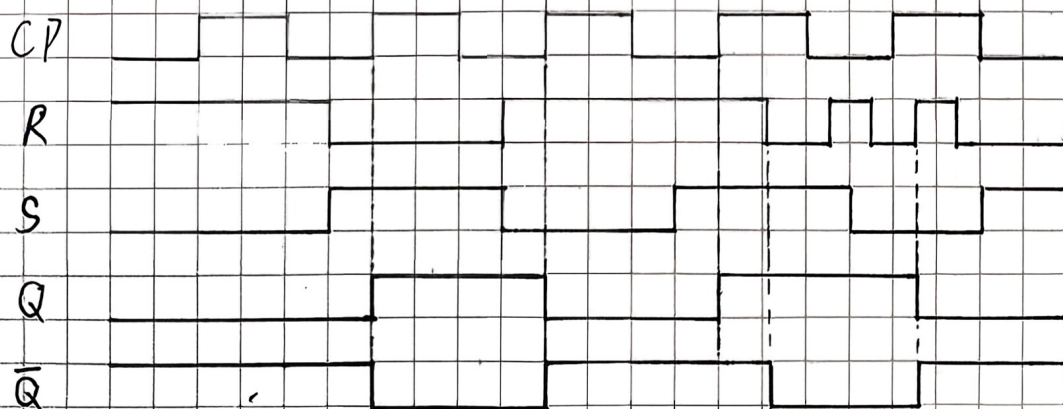4.7 解:


$$\begin{cases} Q_{n+1} = S + \bar{R}Q_n \\ SR = 0 \end{cases}$$



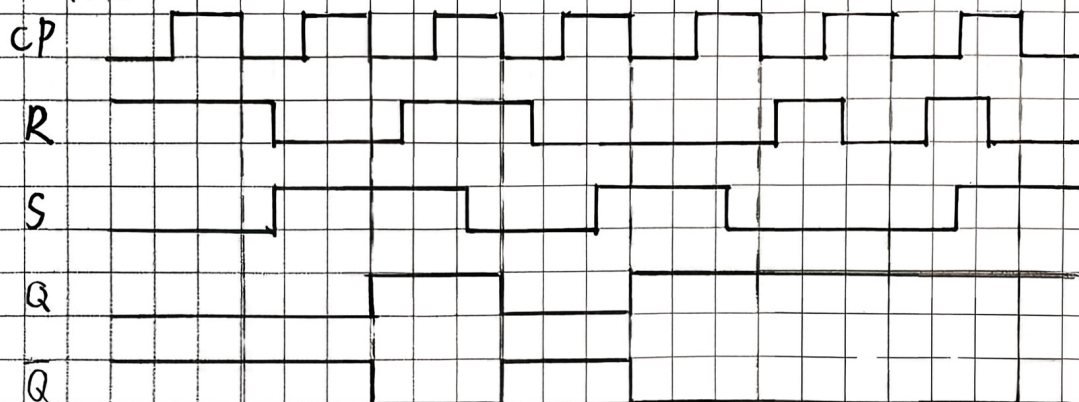4.8


解:

$$\begin{cases} Q_{n+1} = S + \bar{R}Q_n \\ RS = 0 \end{cases}$$



4.10 解:


$$Q_{n+1} = J\bar{Q}_n + KQ_n$$

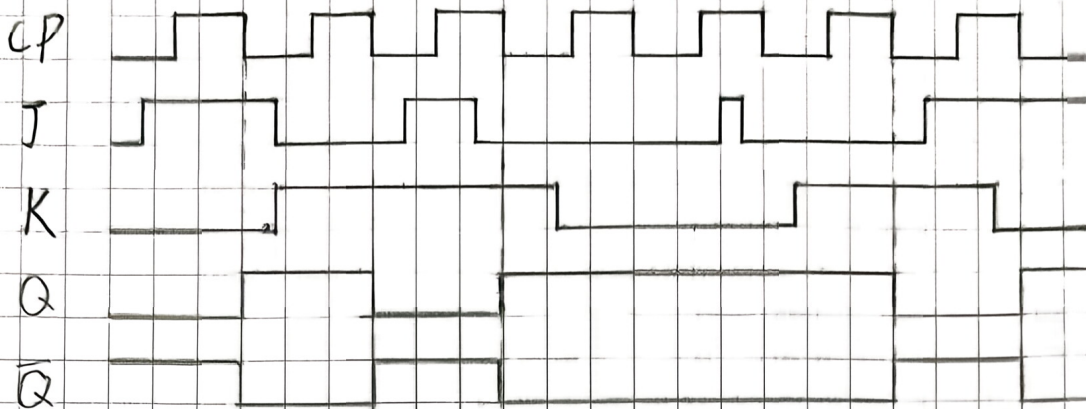

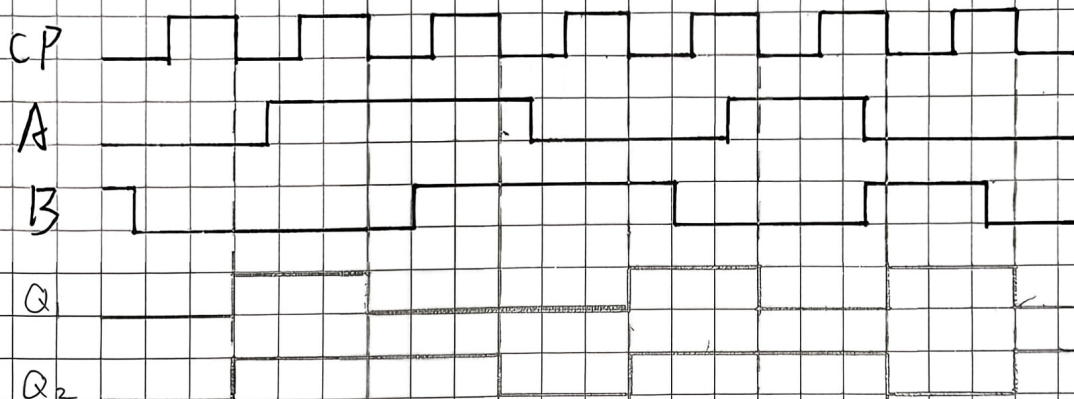
4.11 解:

$$Q_1(n+1) = \bar{A}\bar{B}\bar{Q}_{1n} + \bar{Q}_{1n}Q_{1n} = \bar{A}\bar{B}\bar{Q}_{1n}$$


$$Q_2(n+1) = \bar{A}Q_{2n} + \bar{B}Q_{2n} = \bar{A}\bar{B}Q_{2n}$$



4.12 解:

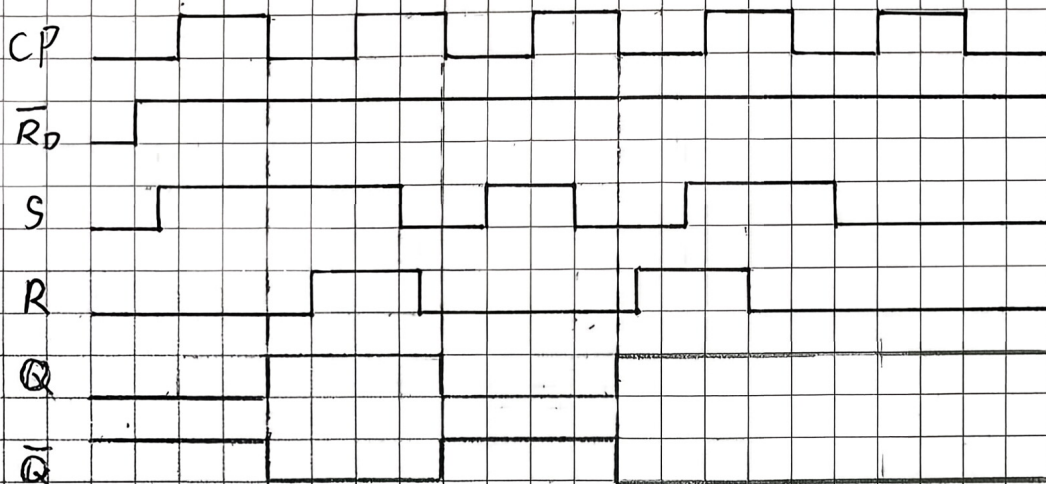


4.13 解:

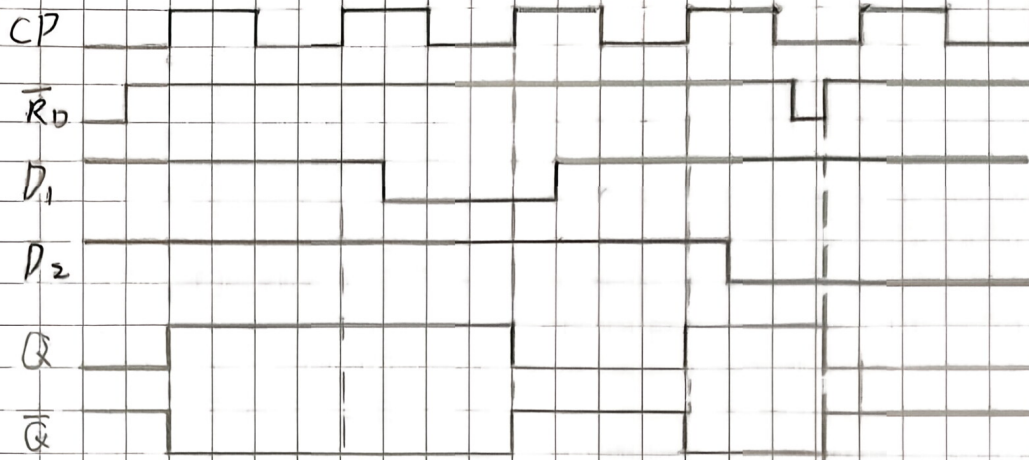

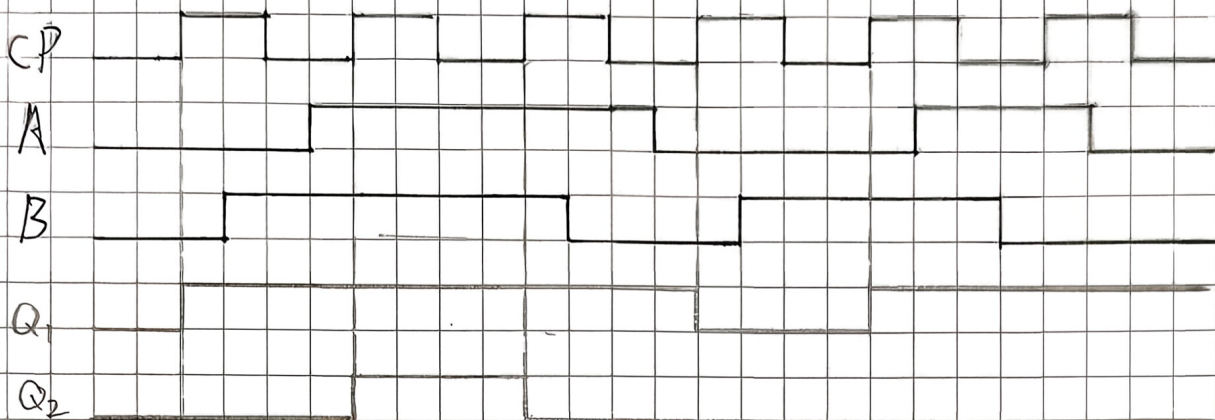4.14 解:

$$Q_{1(n+1)} = A \oplus Q_{1n} \quad Q_{2(n+1)} = B(A \oplus \overline{Q_{2n}})$$



4.15 解:

