

2.2 证明

$$U = E$$

当应变片不受力时, $\Delta R = 0$ 且此时桥路处于平衡状态

因此 $R_1 = R_4$, 设初始平衡状态下 $R_1 = R_4 = R_0$

则 R_1 受拉力时 $R_1 = R_0 + \Delta R$ R_4 受压力时 $R_4 = R_0 + \Delta R$

$$U_{cd} = \frac{R_1}{R_1 + R_2} U - \frac{R_4}{R_4 + R_3} U = \frac{R_1(R_4 + R_3) - R_4(R_1 + R_2)}{(R_1 + R_2)(R_4 + R_3)} U$$

$$= \frac{(R_0 + \Delta R)(R + R_0 - \Delta R) - (R_0 - \Delta R)(R + R_0 + \Delta R)}{(R + R_0 + \Delta R)(R + R_0 - \Delta R)} U$$

$$= \frac{2R\Delta R}{(R + R_0)^2 - \Delta R^2} U = \frac{2R\Delta R}{(R + R_0)^2 - \Delta R^2} E$$

取 $R_0 = R$, 设 $\Delta R^2 \ll R^2$, 上式中 ΔR^2 项可省略, 化为:

$$U_{cd} = \frac{2R\Delta R}{4R^2} E = \left(\frac{E}{2}\right) \left(\frac{\Delta R}{R}\right)$$

2.4 解:

$$m = \frac{R_{\max}}{R_L}$$

当 $m < 0.1$ 时

$$R_L > 10 R_{\max}$$

$$\begin{cases} \delta_2 = 1 - \left[1 - \frac{1}{1 + m'(1-r)} \right] \times \frac{100\%}{100} < 0.1 \\ r = \gamma = \frac{R_x}{R_{\max}} = \frac{1}{2} \quad m' = \frac{R_{\max}}{R_L} \end{cases}$$

$$\text{解得: } m' < \frac{4}{9} \text{ 即 } \frac{R_{\max}}{R_L} < \frac{4}{9} \quad R_{\max} < \frac{4}{9} R_L \quad R_L > \frac{9}{4} R_{\max}$$

2.6 解: 令 $R_x = x R_{\max}$

当 $R_F = 50 \Omega$ 时

$$m_1 = \frac{R_p}{R_F} = 2 \quad r_x = \frac{R_x}{R_{\max}} = x$$

$$y = \frac{r_x}{1 + r_x m_1 (1 - r_x)} = \frac{x}{1 + 2x(1 - x)} \quad x \in \{0, 0.1, 0.2, \dots, 1.0\}$$

x	0	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1.0
y	0	$\frac{5}{59}$	$\frac{5}{33}$	$\frac{5}{71}$	$\frac{10}{49}$	$\frac{10}{37}$	$\frac{15}{37}$	$\frac{35}{71}$	$\frac{20}{33}$	$\frac{45}{59}$	1

当 $R_F = 500 \Omega$ 时

$$m_b = \frac{R_D}{R_F} = \frac{100}{500} = 0.2$$

$$y = \frac{r_x}{1 + m r_x (1 - r_x)} = \frac{x}{1 + 0.2x(1 - x)}$$

$x \in \{0, 0.1, 0.2, \dots, 1.0\}$

x	0	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1.0
y	0	$\frac{50}{509}$	$\frac{25}{129}$	$\frac{150}{521}$	$\frac{50}{131}$	$\frac{10}{21}$	$\frac{74}{131}$	$\frac{350}{521}$	$\frac{100}{129}$	$\frac{450}{509}$	1

2.10 解:

$$\varepsilon_x = \frac{b(1-x)}{W E t^2} \quad F = \frac{b x (0.25 - \frac{0.25}{2})}{0.06 \times 70 \times 10^9 \times (3 \times 10^{-3})^2} \quad x \approx 0.5 \approx 0.1$$

$$\frac{\Delta R}{R_0} = \frac{150}{1000} = 0.15 \quad \Delta R = 0.15 \times 1000 = 150 \Omega$$

$$\Delta R = 0.21 R_0 = 25.2 \Omega$$

$$R_1 = R_3 = R_0 + \Delta R = 145.2 \Omega$$

$$R_2 = R_4 = R_0 - \Delta R = 94.8 \Omega$$